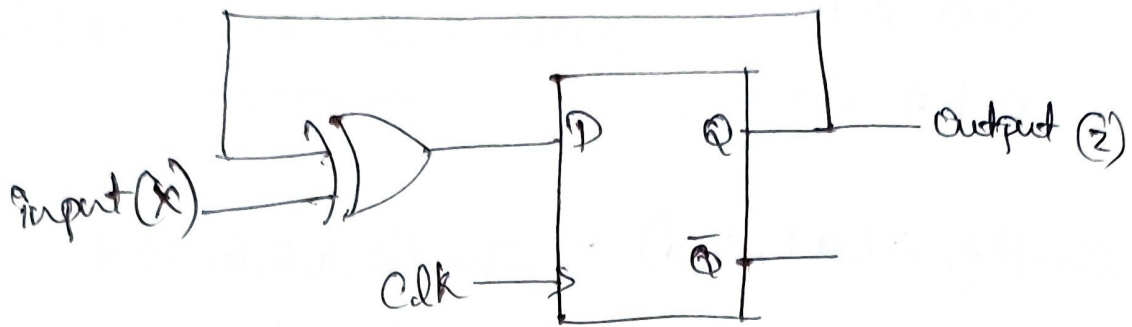


Day 4 Assignment - Sequential

1) Explain the behaviour of the given circuit.



XOR gate inputs are

External input = X

Feedback input = Q

$$D = X \oplus Q$$

$$Q_n = D$$

$$Q_n = X \oplus Q$$

$$Z_n = X \oplus Z$$

State table

Present State (Q)	Input (X)	Q_n
0	0	0
0	1	1
1	0	1
1	1	0

$$\text{Case 1: } X=0 \Rightarrow Q_n = Q$$

$$\text{Case 2: } X=1 \Rightarrow Q_n = \overline{Q}$$

The circuit behaves like a T-Flip Flop.

2) Design a posedge triggered D-FF using 2:1 MUX only Master latch $\Rightarrow M = \text{clk} \uparrow$
 $\text{clk} \downarrow$

Slave latch $\Rightarrow Q = \text{clk} \downarrow M + \overline{\text{clk}} Q$

~~clk = 0.~~

clk = 0.

MUX 1 input

I_0

I_1

select

output

Connection.

D

M (feedback)

clk

m.

clk = 1

MUX 2 input

I_0

I_1

select

Output


Connection.

Q (feedback)

M

clk

Q.

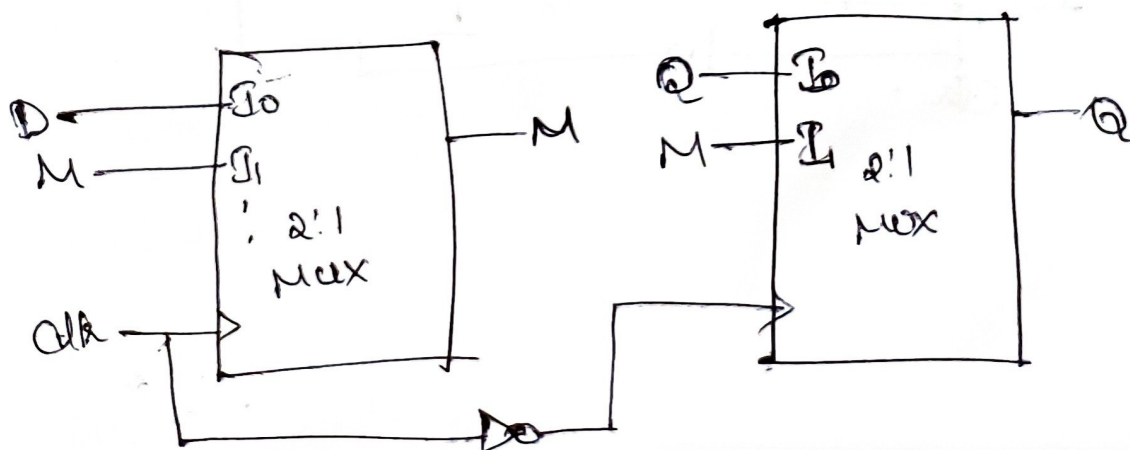

3) Design a negedge triggered T-FF using 2:1 MUX only characteristics equation of T-Flipflop is $Q_{n+1} = T \oplus Q$

For 2:1 MUX

select line - T-Flipflop

$$I_0 = Q$$

$$I_1 = \bar{Q}$$

$$Y = \bar{T}Q + T\bar{Q}$$

$$Y = T \oplus Q$$

$$m = \bar{clk}m + clk(T \oplus m)$$


$$Q = \bar{clk}Q + clk(m)$$

Master latch, $clk = 1$

Input	Connection.
I_0	m (feedback)
I_1	$T \oplus m$
Select	clk
Output	m

Slave latch, $clk = 0$

Input	Connection.
I_0	m
I_1	Q (feedback)
Select	$\bar{clk}$
Output	Q

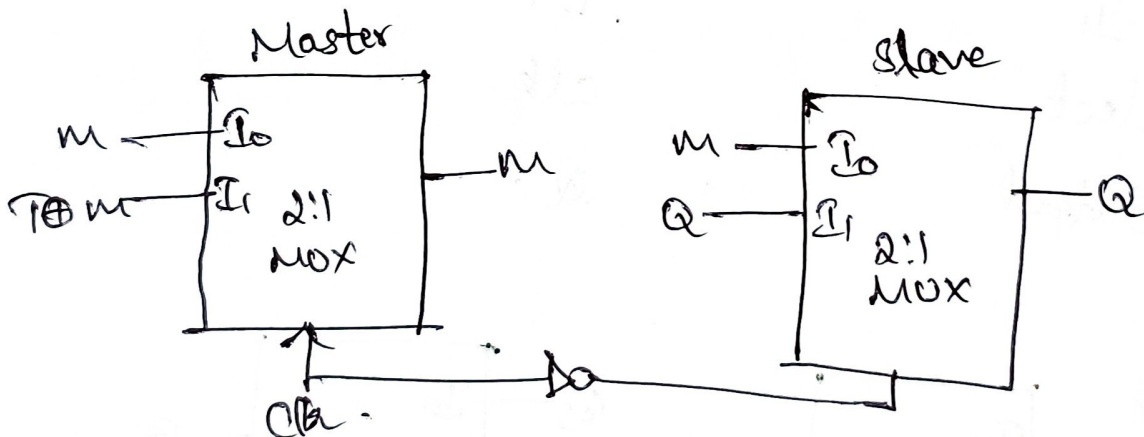


4) Convert by adding external gates:

a) A D-flipflop to a JK flip-flop.

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$


$$Q_{n+1} = D$$

$$D = J\bar{Q}_n + \bar{K}Q_n$$

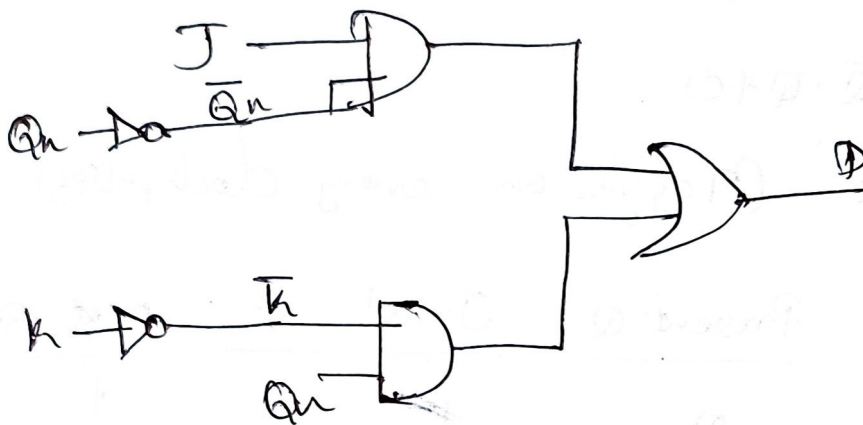


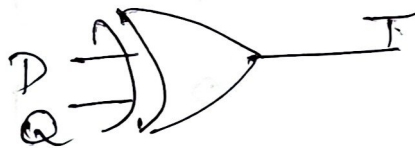b) A T-flipflop to a D-flipflop, $Q_{n+1} = T \oplus Q$

$$Q_{n+1} = D \Rightarrow D = T \oplus Q, T = D \oplus Q$$



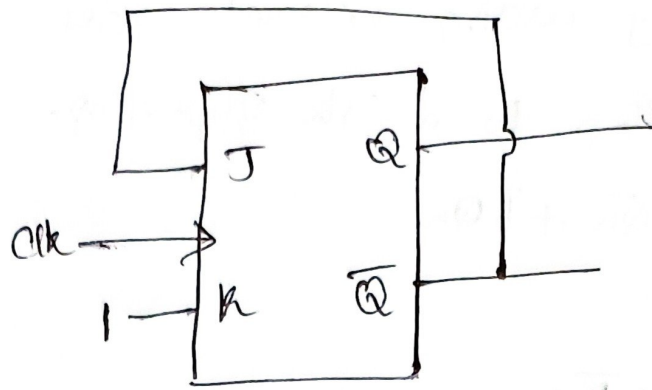5) In a positive edge triggered JK flipflop, we have $J = Q'$ and $K = 1$ as shown in the figure below. Assume the flip flop was initially cleared and then clocked for 6 clock pulses, find the sequences at the output for those 6 clock cycles.



$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

$$K=1 \Rightarrow \bar{K}=0 \quad J=\bar{Q}$$

$$Q_{n+1} = \bar{Q} \cdot Q \neq 0$$

$$Q_{n+1} = \bar{Q} \quad (\text{Toggles on every clock pulse})$$

Clock pulse	Present Q	$J = Q'$	K	next Q.
0	0	1	1	1
1	1	0	1	0
2	0	1	1	1
3	1	0	1	0
4	0	1	1	1
5	1	0	1	0
6	0	1	1	1

Sequence is $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0$